

Bode plot of an RC lowpass filter

